 


Asynchronous Counter: ripple counter.

→ flip flops are always in toggle mode.

(JK, $J=1, K=1$, TFF $\rightarrow T=1$)


→ CLK is applied to only one FF.



Q_0 will toggle at every CLK pulse.

Q_1 will change when Q_0 transits from "1" to "0". "High to low"

Q_2 will change when Q_1 transits from "1" to "0".




	(LSB) Q_0	Q_1	Q_2	(MSB)
-	0	0	0	← 0
1	1	0	0	← 1
2	0	1	0	← 2
3	1	1	0	← 3
4	0	0	1	← 4
5	1	0	1	← 5
6	0	1	1	← 6
7	1	1	1	← 7

mod-8
Counter.

0-1-2-3
-4-5-6
-7-0-

UP
Counter.

 

→ Q_0 will toggle at every clk pulse.


→ Q_1 will change when Q_0 transits from "0" to "1".

→ Q_2 will change when Q_1 transits from "0" to "1".

clk	Q_0	Q_1	Q_2	
—	0	0	0	0
1	1	1	1	7
2.	0	1	1	6
3.	1	0	1	5
4.	0	0	1	4
5.	1	1	0	3
6.	0	1	0	2
7.	1	0	0	1
8.	0	0	0	0

MOD-8
Down
Counter

Type of Counter	edge triggering.	connection of clk. ($Q \rightarrow (+)$, $\bar{Q} \rightarrow (-)$)
UP	-ve	+
down	+ve	+

 

Output freq at first FF $\rightarrow F/2$

(\because because it can count-2)

Output freq at third FF $\rightarrow F/8$

(\because because it can count-8)

max. Input clk frequency

minimum time required to perform proper operation is

$$= N \times t_{pd}$$

N = no. of flip flop

t_{pd} = prop. delay of FF.

$$T \geq N \times t_{pd}$$

$$\frac{1}{T} \leq \frac{1}{N \times t_{pd}}$$

$$f \leq \frac{1}{N \times t_{pd}}$$


$$f_{max} = \frac{1}{N \times t_{pd}}$$

* Construction of Asynchronous Flip Flop.

→ mod-6 OP Counter:

6
0-5

mod-5

 


clk
→ active low
→ NAND
active high
→ AND

clk	Q0	Q1	Q2
1	0	0	0
2	1	0	0
3	0	1	0
4	1	1	0
5	0	0	1
6	1	0	1

↓

6 0 1 - 0 0 0

Q.1

 

Asynchronous

→ (OP.)

→ (-ve) (+ve) → UP Counter. (110)

0 0 0
1 0 0
0 1 0
0 0 0
0 0 0
0 1 0
0 0 0
1 0 0

mod-3 UP counter

1 0 1
0 1 1
1 1 1

